

ELL 201 Group Project Report

Vending Machine

Devesh Yadav 2022MT11281
Piyush Abnave 2022MT11289
Ishant Yadav 2022MT11397
Lokesh Varadraj 2022PH11858

April 2024

1 Introduction

Our topic for this project is An Ideal Vending Machine. A vending machine is an automated machine that dispenses items such as snacks, beverages, cigarettes and lottery tickets to consumers after cash, a credit card, or other forms of payment are inserted into the machine. The vending machine we designed for this project is an ideal machine(explained in the "Working of the Machine" section).

2 Concepts Used

The project is based on the concept of a clocked synchronous digital Finite State Machine (FSM). The FSM can change from one state to another in response to some inputs. The change from one state to another is called a transition. The FSM we use here is the Mealy Machine. Mealy Machine is a finite state machine whose output values are determined solely by its current state and inputs. We make use of a state transition diagram. The Mealy Machine State Diagram gives two outputs; one signifies the state it is going to, and the other signifies the output it gives at the initial state. The Mealy FSM is used to make vending machines.

3 Working of The Machine

The only denominations our vending machine accepts are 5 Rs and 10 Rs. The machine can only accept up to 15 Rs, which signifies the complete transaction. The machine also gives back the change after each transaction. Following is the state diagram of our machine:

 


Figure 1: State Diagram

We have three states: S0 for 0 Rs, S1 for 5 Rs and S2 for 10 Rs. We require 15 Rs for a complete transaction. We transition between states depending on the input we give at any state (5 Rs or 10 Rs). A reset button is also present to reset the model, which takes us back to the 0 Rs state. We get two outputs. One output signifies the completion of a transaction, i.e. when the system receives 15 Rs or more than 15 Rs. This is signified by the ignition of one LED. In case the system receives more than 15 Rs (For example, the system has 10 Rs in it, and we input another 10 Rs into it), the necessary change is signified by two LEDs, one for 5 Rs change and the other for 10 Rs change. The vending machine we designed is also ideal: for example, if we input 10 Rs into the machine and don't wish to transact further, the machine returns us the 10 Rs in the form of change by displaying it in the output. In this way, transactions are done.

4 Characteristic Equations

Two-bit inputs are given into the system. The inputs are of three types, 0 Rs, 5 Rs and 10 Rs, as mentioned below:

Decoding	
Inputs	X1,X0
0 Rs	0 0
5 Rs	0 1
10 Rs	1 0

Figure 2: Inputs

Three-bit outputs are received. One output signifies when the transaction is complete. The other two outputs signify the change received from the machine (5 Rs or 10 Rs). They are shown as follows:

Outputs	Y2
Not Vent	0
Vent	1
Output(Changes given out by machine)	Y1,Y0
0 Rs	0 0
5 Rs	0 1
10 Rs	1 0

Figure 3: Outputs

In accordance with the inputs and the outputs, the state excitation table can be given as follows:

Current State		Next State			Output (Corresponding to next state in previous column)	
Inputs	0 Rs	5 Rs	10 Rs	0 Rs	5 Rs	10 Rs
0 0	0 0	0 1	1 0	NV,0	NV,0	NV,0
0 1	0 0	1 0	0 0	NV,5	NV,0	V,0
1 0	0 0	0 0	0 0	NV,10	V,0	V,5

Figure 4: State Excitation Table

For this project, our flip-flop choice is the D flip-flop. The conversion to D flip-flop of the Mealy FSM is shown as follows:

Inputs	Previous States	Next States	Flip Flop Inputs	Outputs
X1,X0	Q1,Q2	Q1+,Q0+	D1,D0	Y2,Y1,Y0
0 0	0 0	0 0	0 0	0 0 0
0 0	0 1	0 0	0 0	0 0 1
0 0	1 0	0 0	0 0	0 1 0
0 1	0 0	0 1	0 1	0 0 0
0 1	0 1	1 0	1 0	0 0 0
0 1	1 0	0 0	0 0	1 0 0
1 0	0 0	1 0	1 0	0 0 0
1 0	0 1	0 0	0 0	1 0 0
1 0	1 0	0 0	0 0	1 0 1

Figure 5: Conversion to D Flip-Flop

We now write the characteristic equations for D0, D1, Y0, Y1 and Y2, respectively. The K-Maps and their characteristic equations are as follows:

		D0 Kmap			
X1,X0	Q1,Q0	0 0	0 1	1 1	1 0
	0 0	0	0	0	0
	0 1	1	0	0	0
	1 1	X	X	X	X
	1 0	0	0	0	0
$D0=X0.Q1'.Q0'$					

Figure 6: K-Map for D0

		D1 Kmap			
X1,X0	Q1,Q0	0 0	0 1	1 1	1 0
	0 0	0	0	0	0
	0 1	0	1	0	0
	1 1	X	X	X	X
	1 0	1	0	0	0
$D1=X1.Q1'.Q0'+X0.Q1'.Q0$					

Figure 7: K-Map for D1

		Y0 Kmap			
Q1,Q0					
X1,X0		0 0	0 1	1 1	1 0
0 0		0	1	0	0
0 1		0	0	0	0
1 1		X	X	X	X
1 0		0	0	0	1
Y0=X1'.X2'Q1'.Q0+X1.Q1.Q0'					

Figure 8: K-Map for Y0

		Y1 Kmap			
Q1,Q0					
X1,X0		0 0	0 1	1 1	1 0
0 0		0	0	0	1
0 1		0	0	0	0
1 1		X	X	X	X
1 0		0	0	0	0
Y1=X1'.X0'.Q1.Q0'					

Figure 9: K-Map for Y1

		Y2 Kmap			
Q1,Q0					
X1,X0 \	0 0	0 1	1 1	1 0	
0 0	0	0	0	0	
0 1	0	0	0	1	
1 1	X	X	X	X	
1 0	0	1	0	1	
$Y2=X1.Q1'.Q0+X0.Q1.Q0'+X1.Q1.Q0'$					

Figure 10: K-Map for Y2

5 Verilog Code and Waveforms

The following is the Verilog Code:

```
design.sv
1 module vending_machine(
2   input clk,
3   input rst,
4   input [1:0] in, // 01 = 5 rs, 10 = 10 rs
5   output reg out,
6   output reg [1:0] change
7 );
8 parameter s0 = 2'b00;
9 parameter s1 = 2'b01;
10 parameter s2 = 2'b10;
11
12 reg[1:0] c_state, n_state;
13
14 always @ (posedge clk)
15 begin
16   if(rst == 1)
17   begin
18     c_state = 0;
19     n_state = 0;
20     change = 2'b00;
21   end
22   else
23     c_state = n_state;
24
25   case(c_state)
26     s0: // state 0 : 0 rs
27       if(in == 0 )
28       begin
29         n_state = s0;
30         out = 0;
31         change = 2'b00;
32       end
33     else if(in == 2'b01)
34     begin
35       n_state = s1;
36       out = 0 ;
37       change = 2'b00;
38     end
39     else if(in == 2'b10)
40     begin
41       n_state = s2;
42       out = 0;
43       change = 2'b00;
44     end
45     s1: //state 1: 5rs
46       if(in == 0 )
47       begin
48         n_state = s0;
49         out = 0;
50         change = 2'b01; // change returned 5rs
51       end
52   end
53 end
```



```

50         change = 2'b01; // change returned 5rs
51     end
52 else if (in == 2'b01)
53     begin
54         n_state = s2;
55         out = 0;
56         change = 2'b00;
57     end
58 else if(in == 2'b10)
59     begin
60         n_state = s0;
61         out = 1;
62         change = 2'b00;
63     end
64 s2:// state2: 10 rs
65 if(in == 0)
66     begin
67         n_state = s0;
68         out = 0;
69         change = 2'b10;
70     end
71 else if(in == 2'b01)
72     begin
73         n_state = s0;
74         out = 1;
75         change = 2'b00;
76     end
77 else if( in == 2'b10)
78     begin
79         n_state = s0;
80         out = 1;
81         change = 2'b01; // change returned 5rs and 1 bottle
82     end
83 endcase
84 end
85 endmodule
86

```

We make a module vending machine and declare our variables there. Our input and outputs are decoded as used in the characteristic equation. Out is for y2, change[0]=y1 and change[0]=y0. Three parameters are declared, denoting the states. Then, the current state and next state are stored in some variables. Then, a loop begins for every positive clock edge. According to the current state of the Mealy machine, s0, s1 or s2 cases are defined. Inside the cases, according to the state transition diagram, if-else conditions are used to define the transitions of the machine from one state to another.

The testbench used is as follows:


```

testbench.v
5  reg rst;
6
7  // Outputs
8  wire out;
9  wire [1:0] change;
10 wire [1:0] c_state;
11 wire [1:0] n_state;
12
13 // Instantiate the unit under test
14 vending_machine uut (
15     .clk(clk),
16     .rst(rst),
17     .in(in),
18     .out(out),
19     .change(change)
20 );
21
22 // Clock generation
23 always #5 clk = ~clk; // Toggle the clock every 5 time units
24
25 // Monitor c_state and n_state
26 always @(posedge clk) begin
27     $display("At time %t: c_state = %b, n_state = %b", $time, c_state,
28 n_state);
29 end
30
31 // Test case
32 initial begin
33     // Initialize inputs
34     rst = 1;
35     clk = 0;
36     in = 0;
37
38     // Dump waveform
39     $dumpfile("vending_machine.vcd");
40     $dumpvars(0, vending_machine_tb);
41
42     // Release reset and start clock
43     #6 rst = 0;
44
45     // Input sequence
46     #5; // Wait for 5 time units
47     in = 1; // Input turned on at time 11
48     #5 in = 1; // Input turned on at time 16
49     #10; // Wait for additional 10 time units
50
51     // Finish simulation
52     #100 $finish;
53 end
endmodule

```


First, we initialise the inputs and output ports needed. Then, the module for the testbench is defined. Inside the module, reset is set to 1 at 0 time so that the garbage values are erased. At the 6 time, the unit reset is turned off. The input of $y1 = 0$, $y0 = 1$, i.e. 5 Rs, is given. Then, at intervals of 5 times, a unit input of 0.1 (5 Rs) is again given twice. One at 16 sec and the other at 25 seconds. So, This represents the case where 5 Rs is given 3 times. So, the transaction is complete. Out for venting machine gives output 1, and no changes are returned. This represents that the machine goes from state s0 to s2 to s3 and finally to s0. After that, the simulation is stopped.

The waveform obtained is as follows:

 

You can see that when the machine's state was changed, we added red circles. The `n_state` variable is changed from 0 to 1 and then 3. At 3, the transition is complete. So the `out` wave becomes 1. The `change` waves remain zero all the time as no changes are given out in our example.

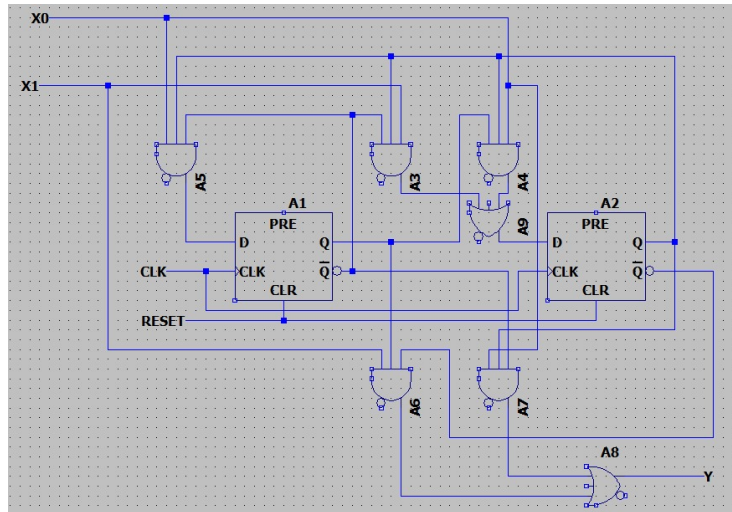The following is the circuit diagram for our Verilog code. Please note that only the Y1 output is shown due to the complexity issue of our diagram (the diagram was too large in size).



6 Conclusion

In this way, our project for a vending machine was modelled using an FSM and realised on a CPLD board using Verilog. The K-Maps and characteristic equations were made. The Verilog Code, its implementation, the waveform received and the circuit diagram are explained.